

# PWM & 555 Timer

## The Basics of PWM and 555 Timer Circuits

Zachariadis Charalampos & Vrakatselis Christos

Starbound Team  
IEEE University of Thessaly SB

November 28, 2024



① Intro

② Square Signals

③ Outro

### Description

## Internal Circuit

## Pros & Cons

## 2 Square Signals

### 3 Outro

## 1 Intro

Description

Internal Circuit

Pros & Cons

## 2 Square Signals

## 3 Outro

# Description

- The 555 timer gets its name from the fact that there are three internally connected 5k resistors which it uses to generate the two comparators reference voltages. It is a highly stable device for generating accurate time delays or oscillation. Additional terminals are provided for triggering or resetting if desired.

# Description

- The 555 timer gets its name from the fact that there are three internally connected 5k resistors which it uses to generate the two comparators reference voltages. It is a highly stable device for generating accurate time delays or oscillation. Additional terminals are provided for triggering or resetting if desired.
- In the time delay mode of operation, the time is precisely controlled by one external resistor and capacitor. For a stable operation as an oscillator, the free running frequency and duty cycle are accurately controlled with two external resistors and one capacitor. And here is the connection between PWM and the 555 Timer!

# Description

- The 555 timer gets its name from the fact that there are three internally connected 5k resistors which it uses to generate the two comparators reference voltages. It is a highly stable device for generating accurate time delays or oscillation. Additional terminals are provided for triggering or resetting if desired.
- In the time delay mode of operation, the time is precisely controlled by one external resistor and capacitor. For a stable operation as an oscillator, the free running frequency and duty cycle are accurately controlled with two external resistors and one capacitor. And here is the connection between PWM and the 555 Timer!
- The circuit may be triggered and reset on falling waveforms, and the output circuit can source or sink up to 200 mA or drive TTL circuits.

## 1 Intro

Description

Internal Circuit

Pros & Cons


## 2 Square Signals

## 3 Outro



# Pin Configuration and Functions

| No. | Name            | Description   |
|-----|-----------------|---|
| 1   | GND             | Ground reference voltage.   |
| 2   | Trigger         | Responsible for transition of the flip-flop from set to reset.                          |
| 3   | Output          | Output driven waveform.   |
| 4   | Reset           | Negative pulse applied to this pin to disable or reset the timer (!R1 – Master Reset).  |
| 5   | Control Voltage | Controls the threshold and trigger levels.  |
| 6   | Threshold       | Compares the voltage applied to the terminal with a reference voltage of $2/3 V_{CC}$ . |
| 7   | Discharge       | Open collector output which discharges a capacitor between intervals.                   |
| 8   | $V^+$           | Supply voltage with respect to GND.   |

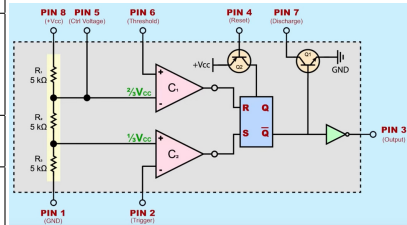

## 1 Intro

Description

Internal Circuit

Pros & Cons

## 2 Square Signals

## 3 Outro

# Pros & Cons

- The NE555 chip is very cheap to produce.

# Pros & Cons

- The NE555 chip is very cheap to produce.
- We can easily configure it in different ways, with just a several passive elements.

## Pros & Cons

- The NE555 chip is very cheap to produce.
- We can easily configure it in different ways, with just a several passive elements.
- The times of generated pulses do not depend on the supply voltage.

# Pros & Cons

- The NE555 chip is very cheap to produce.
- We can easily configure it in different ways, with just a several passive elements.
- The times of generated pulses do not depend on the supply voltage.
- High current consumption.

# Pros & Cons

- The NE555 chip is very cheap to produce.
- We can easily configure it in different ways, with just a several passive elements.
- The times of generated pulses do not depend on the supply voltage.
- High current consumption.
- Extended first impulse in relation to the others. This is due to the need to charge the capacitor from zero, while later it is discharged to  $1/3$  of the supply voltage.

# Pros & Cons

- The NE555 chip is very cheap to produce.
- We can easily configure it in different ways, with just a several passive elements.
- The times of generated pulses do not depend on the supply voltage.
- High current consumption.
- Extended first impulse in relation to the others. This is due to the need to charge the capacitor from zero, while later it is discharged to  $1/3$  of the supply voltage.
- The NE555 is not suitable for precise measuring of very long times.



## Pros & Cons

- The NE555 chip is very cheap to produce.
- We can easily configure it in different ways, with just a several passive elements.
- The times of generated pulses do not depend on the supply voltage.
- High current consumption.
- Extended first impulse in relation to the others. This is due to the need to charge the capacitor from zero, while later it is discharged to  $1/3$  of the supply voltage.
- The NE555 is not suitable for precise measuring of very long times.
- On the other side, we can obtain only 500kHz or slightly more.

## 1 Intro

## 2 Square Signals

Monostable Mode

Bistable Mode

Astable Mode

## 3 Outro

1 Intro

2 Square Signals

- Monostable Mode
- Bistable Mode
- Astable Mode

3 Outro


# Description

- A monostable multivibrator is basically an electronic device having only one stable state out of the two possible logic states: HIGH or LOW.

# Description

- A monostable multivibrator is basically an electronic device having only one stable state out of the two possible logic states: HIGH or LOW.
- When a monostable multivibrator is triggered externally, it produces a single output pulse in the unstable state for a short duration and then returns back to the stable state.

# Basic Circuit

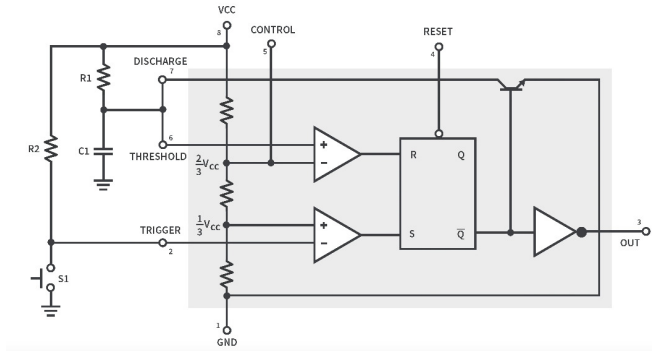

# Basic Circuit

- A resistor is connected between VCC and the common node of threshold (6) and discharge pin (7), and a capacitor is connected between the common node and ground. The voltage across the capacitor acts like input for the threshold and discharge pin.

# Basic Circuit

- A resistor is connected between VCC and the common node of threshold (6) and discharge pin (7), and a capacitor is connected between the common node and ground. The voltage across the capacitor acts like input for the threshold and discharge pin.
- An external switch is connected to the trigger pin (2) of the timer via a pull-up network, and it is used to control the output of the timer.



# Basic Circuit

- A resistor is connected between VCC and the common node of threshold (6) and discharge pin (7), and a capacitor is connected between the common node and ground. The voltage across the capacitor acts like input for the threshold and discharge pin.
- An external switch is connected to the trigger pin (2) of the timer via a pull-up network, and it is used to control the output of the timer.
- The reset pin (4) of the IC is connected to VCC to avoid any accidental resets during the operation.

# Basic Circuit

- A resistor is connected between VCC and the common node of threshold (6) and discharge pin (7), and a capacitor is connected between the common node and ground. The voltage across the capacitor acts like input for the threshold and discharge pin.
- An external switch is connected to the trigger pin (2) of the timer via a pull-up network, and it is used to control the output of the timer.
- The reset pin (4) of the IC is connected to VCC to avoid any accidental resets during the operation.
- The control voltage pin (5) is connected to the ground via a small capacitor to avoid noise when not in use.

# Output Configurations

- In the monostable mode of the 555 timer, also known as the "one-shot mode", when we apply a logic LOW to the trigger pin of the timer by closing the switch, the output becomes logic HIGH and holds there for a specific time duration (T).

# Output Configurations


- In the monostable mode of the 555 timer, also known as the "one-shot mode", when we apply a logic LOW to the trigger pin of the timer by closing the switch, the output becomes logic HIGH and holds there for a specific time duration (T).
- This time period T is calculated by the following relation:

$$T = 1.1 \cdot R \cdot C$$

where R is in Ohms and C is in Farads.

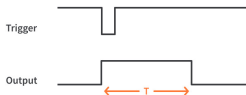
# Output Configurations

- After the time period  $T$ , the output again falls back to logic LOW and waits for the next trigger:



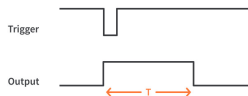
# Output Configurations

- After the time period  $T$ , the output again falls back to logic LOW and waits for the next trigger:



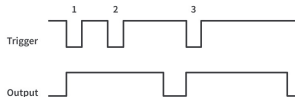- If another event is triggered during a previous event when the output pulse is high, it'll simply not respond to the trigger. As you can see below, we get an output pulse due to the 1st and 3rd trigger pulse but the 2nd trigger pulse is simply ignored:



## Internal Operation

# Why is this all happening?

To see what's under the hood you should visit the following article in the senction "Internal Operation as a Monostable Multivibrator":

[https://www.circuitbread.com/tutorials/  
555-timer-2-monostable-multivibrator-configuration](https://www.circuitbread.com/tutorials/555-timer-2-monostable-multivibrator-configuration)

# Basic Applications

- **Debouncing Switches:** When a switch is pressed, it can produce multiple transitions (bounces) before settling, with the monostable mode we can generate a single clean pulse, thus eliminating the noise from the bouncing.



# Basic Applications

- **Debouncing Switches:** When a switch is pressed, it can produce multiple transitions (bounces) before settling, with the monostable mode we can generate a single clean pulse, thus eliminating the noise from the bouncing.
- **Time Delay Generation:** It can be used to create precise time delays in circuits. Once triggered, it will produce a pulse of a defined duration, which is useful in applications requiring a delay, such as delay before turning on/off devices.

# Basic Applications

- **Debouncing Switches:** When a switch is pressed, it can produce multiple transitions (bounces) before settling, with the monostable mode we can generate a single clean pulse, thus eliminating the noise from the bouncing.
- **Time Delay Generation:** It can be used to create precise time delays in circuits. Once triggered, it will produce a pulse of a defined duration, which is useful in applications requiring a delay, such as delay before turning on/off devices.
- **Pulse Shaping:** It can be used to condition or shape pulses in digital circuits. For instance, it can convert a noisy or irregular pulse into a clean, consistent output pulse.

# Basic Applications

- **Debouncing Switches:** When a switch is pressed, it can produce multiple transitions (bounces) before settling, with the monostable mode we can generate a single clean pulse, thus eliminating the noise from the bouncing.
- **Time Delay Generation:** It can be used to create precise time delays in circuits. Once triggered, it will produce a pulse of a defined duration, which is useful in applications requiring a delay, such as delay before turning on/off devices.
- **Pulse Shaping:** It can be used to condition or shape pulses in digital circuits. For instance, it can convert a noisy or irregular pulse into a clean, consistent output pulse.
- **Capacitive Touch Sensors:** Monostable mode can be used in touch-sensitive applications where touching a sensor produces a pulse that can trigger other actions.

## 1 Intro

## 2 Square Signals

Monostable Mode

**Bistable Mode**

Astable Mode

## 3 Outro

# Description

- A bistable multivibrator is an electronic device with two stable states. That means the circuit stays at either of the two states, HIGH or LOW unless externally triggered to switch between them.


# Description

- A bistable multivibrator is an electronic device with two stable states. That means the circuit stays at either of the two states, HIGH or LOW unless externally triggered to switch between them.
- We need a second trigger to make it return to its original stable state, i.e., it doesn't return automatically. This is the main difference between a monostable and a bistable multivibrator.

# Description

- A bistable multivibrator is an electronic device with two stable states. That means the circuit stays at either of the two states, HIGH or LOW unless externally triggered to switch between them.
- We need a second trigger to make it return to its original stable state, i.e., it doesn't return automatically. This is the main difference between a monostable and a bistable multivibrator.
- It's the simplest and least popular mode since it has little applications and you can just replace it with a simpler latching switch which can do the same job.

# Basic Circuit

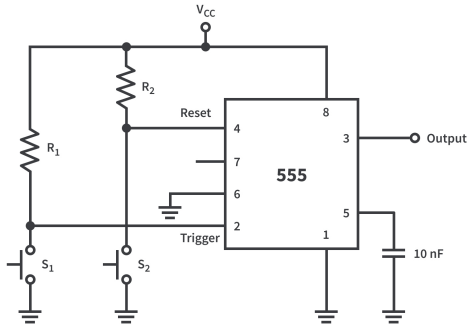



# Basic Circuit

- The first pull-up network, made using the resistor R1 and switch S1 is connected to the trigger pin (2) of the timer.

# Basic Circuit

- The first pull-up network, made using the resistor R1 and switch S1 is connected to the trigger pin (2) of the timer.
- The second pull-up network consisting of R2 and S2 is connected to the reset pin (4) of the timer. The reset pin is an active low pin so the flip flop is reset only when a logic LOW is applied to the pin.

## Basic Circuit

- The first pull-up network, made using the resistor R1 and switch S1 is connected to the trigger pin (2) of the timer.
- The second pull-up network consisting of R2 and S2 is connected to the reset pin (4) of the timer. The reset pin is an active low pin so the flip flop is reset only when a logic LOW is applied to the pin.
- The control pin (5) is connected to the ground through a 10nF capacitor.

## Basic Circuit

- The first pull-up network, made using the resistor R1 and switch S1 is connected to the trigger pin (2) of the timer.
- The second pull-up network consisting of R2 and S2 is connected to the reset pin (4) of the timer. The reset pin is an active low pin so the flip flop is reset only when a logic LOW is applied to the pin.
- The control pin (5) is connected to the ground through a 10nF capacitor.
- We simply leave the discharge pin (7) of the timer unconnected because in this mode of operation there isn't any capacitor to charge or discharge.

# Basic Circuit

- The first pull-up network, made using the resistor R1 and switch S1 is connected to the trigger pin (2) of the timer.
- The second pull-up network consisting of R2 and S2 is connected to the reset pin (4) of the timer. The reset pin is an active low pin so the flip flop is reset only when a logic LOW is applied to the pin.
- The control pin (5) is connected to the ground through a 10nF capacitor.
- We simply leave the discharge pin (7) of the timer unconnected because in this mode of operation there isn't any capacitor to charge or discharge.
- The threshold pin is grounded in this mode to avoid accidental reset due to the R input of the flip flop.

# Output Configurations

- The figure below represents the complete output waveform of the bistable mode of the 555 timers. You can see in the figure that the output switches to HIGH when the trigger is pulled LOW, and the output switches back to LOW when the reset pin is pulled LOW:



## Internal Operation

# Why is this all happening?

To see what's under the hood you should visit the following article in the section "Internal Operation as a Bistable Multivibrator":

[https://www.circuitbread.com/tutorials/  
555-timer-3-bistable-multivibrator-configuration](https://www.circuitbread.com/tutorials/555-timer-3-bistable-multivibrator-configuration)

# Basic Applications

- **Push-button Toggle:** It can create a toggle switch, where a single push-button can turn a device on or off. Each press of the button changes the state of the output.



# Basic Applications

- **Push-button Toggle:** It can create a toggle switch, where a single push-button can turn a device on or off. Each press of the button changes the state of the output.
- **Simple Memory Element:** It can act as a simple memory element in digital circuits, storing the state of a single bit of information.

# Basic Applications

- **Push-button Toggle:** It can create a toggle switch, where a single push-button can turn a device on or off. Each press of the button changes the state of the output.
- **Simple Memory Element:** It can act as a simple memory element in digital circuits, storing the state of a single bit of information.
- **Frequency Divider (as each mode):** By triggering the 555 timer with a high-frequency signal and adjusting the pulse width, the output will have a lower frequency.

## 1 Intro

## 2 Square Signals

Monostable Mode

Bistable Mode

Astable Mode

## 3 Outro


# Description

- An astable multivibrator is an electronic device with no stable state, i.e., it continuously oscillates between the two states HIGH and LOW. It is also known as a free-running multivibrator.

# Description

- An astable multivibrator is an electronic device with no stable state, i.e., it continuously oscillates between the two states HIGH and LOW. It is also known as a free-running multivibrator.
- As we saw in the previously, the monostable and the bistable multivibrator need an external trigger for their operation. But an astable multivibrator is different as it doesn't need any external trigger pulse. It has a built-in automatic triggering to switch between the states.

# Basic Circuit

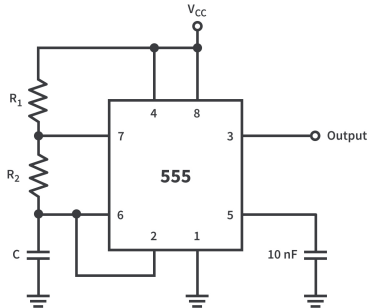

## Basic Circuit

- The threshold pin (6) and trigger pin (2) are connected together. So at any instant, both the pins will receive the same input.

# Basic Circuit

- The threshold pin (6) and trigger pin (2) are connected together. So at any instant, both the pins will receive the same input.
- The external capacitor is connected between the ground and the common node of the threshold and trigger pin.



## Basic Circuit

- The threshold pin (6) and trigger pin (2) are connected together. So at any instant, both the pins will receive the same input.
- The external capacitor is connected between the ground and the common node of the threshold and trigger pin.
- The discharge pin (7) is connected to a node between the two external resistors.

# Basic Circuit

- The threshold pin (6) and trigger pin (2) are connected together. So at any instant, both the pins will receive the same input.
- The external capacitor is connected between the ground and the common node of the threshold and trigger pin.
- The discharge pin (7) is connected to a node between the two external resistors.
- The reset pin (4) is pulled high to avoid accidental resets.

# Basic Circuit

- The threshold pin (6) and trigger pin (2) are connected together. So at any instant, both the pins will receive the same input.
- The external capacitor is connected between the ground and the common node of the threshold and trigger pin.
- The discharge pin (7) is connected to a node between the two external resistors.
- The reset pin (4) is pulled high to avoid accidental resets.
- The control pin (5) can be used to change the threshold reference voltage of  $V_{CC}$ . We can apply external voltage on this pin and the reference voltage can be changed to values other than  $V_{CC}$ . However, here we will not be changing the reference voltage so the control pin is grounded via a 10nF capacitor.

# Output Configurations

- The duration for which the capacitor is charging up to  $\frac{2}{3}V_{CC}$  us how much we get a logic HIGH at the output for every period. We can calculate it with this formula:

$$T = 0.693 \cdot (R_1 + R_2) \cdot C$$

# Output Configurations

- The duration for which the capacitor is charging up to  $\frac{2}{3}V_{CC}$  us how much we get a logic HIGH at the output for every period. We can calculate it with this formula:

$$T = 0.693 \cdot (R_1 + R_2) \cdot C$$

- The timer outputs a logic LOW for the duration that the capacitor is discharging. We calculate it using this formula:

$$T = 0.693 \cdot R_2 \cdot C$$

# Output Configurations

- The duration for which the capacitor is charging up to  $\frac{2}{3}V_{CC}$  is how much we get a logic HIGH at the output for every period. We can calculate it with this formula:

$$T = 0.693 \cdot (R_1 + R_2) \cdot C$$


- The timer outputs a logic LOW for the duration that the capacitor is discharging. We calculate it using this formula:

$$T = 0.693 \cdot R_2 \cdot C$$

- It's highly recommended to use high resistances so that the resistance of the BJT transistor doesn't affect the RC calculations. For more details you can check [this video](#).

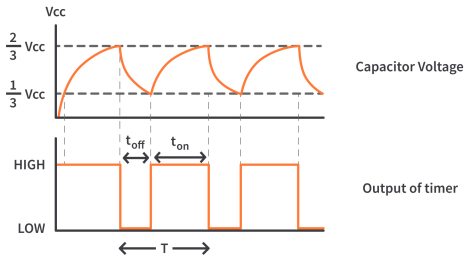
# Output Configurations

- Below is the complete waveform of the astable mode of the 555 timers along with the voltage across the capacitor:


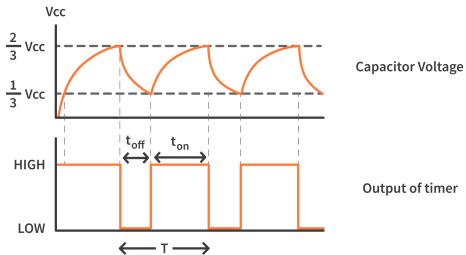
# Output Configurations

- Below is the complete waveform of the astable mode of the 555 timers along with the voltage across the capacitor:



- We the help of the formulas and the image we can easily realise that always:  $t_{off} < t_{on}$  and  $T_{period} = t_{on} + t_{off}$ .



# Internal Operation

## Why is this all happening?

To see what's under the hood you should visit the following article in the senction "Internal Operation as a Astable Multivibrator":

<https://www.circuitbread.com/tutorials/555-timer-4-astable-multivibrator-configuration>

# Basic Applications

- **Clock Generation:** Astable mode can be used to generate clock pulses for digital circuits. These clock pulses can be used for timing purposes, such as in counters, registers, and flip-flops.

# Basic Applications

- **Clock Generation:** Astable mode can be used to generate clock pulses for digital circuits. These clock pulses can be used for timing purposes, such as in counters, registers, and flip-flops.
- **Pulse Width Modulation (PWM):** It's the most popular mode for creating PWM signals to control the brightness of LEDs, speed of motor, etc.

# Basic Applications

- **Clock Generation:** Astable mode can be used to generate clock pulses for digital circuits. These clock pulses can be used for timing purposes, such as in counters, registers, and flip-flops.
- **Pulse Width Modulation (PWM):** It's the most popular mode for creating PWM signals to control the brightness of LEDs, speed of motor, etc.
- **Tone Generation:** It can generate audio tones for various applications, including alarms, sound effects, and simple music instruments.

1 Intro

2 Square Signals

3 Outro

- [https://www.electronics-tutorials.ws/waveforms/555\\_timer.html](https://www.electronics-tutorials.ws/waveforms/555_timer.html)
- <https://www.ti.com/lit/ds/symlink/lm555.pdf>
- <https://fulmanski.pl/tutorials/electronics/introduction/555-2/>
- <https://www.circuitbread.com/tutorials/555-timer-2-monostable-multivibrator-configuration>
- <https://www.circuitbread.com/tutorials/555-timer-3-bistable-multivibrator-configuration>
- <https://www.circuitbread.com/tutorials/555-timer-4-astable-multivibrator-configuration>

*Thanks For Your Attention!*  
Any questions?